

## 02 – TRANSISTORS TO GATES

COMP256 – COMPUTING ABSTRACTIONS  
DICKINSON COLLEGE

## COMP256 – COMPUTING ABSTRACTIONS

- Prof. Grant Braught
  - <http://users.dickinson.edu/~braught/>
  - Office hours, Meetings, Course Link
- Syllabus or Course Questions?


## TRANSISTORS AS SWITCHES

- Transistors are electronic components that can behave as *electrically controlled switches*.
- Transistors are *solid-state* (i.e. no moving parts) devices.
- There are two basic types of transistors, *N-Type* and *P-Type*.
  - Different switching behavior is produced by impurities added to the silicon dioxide semiconductor during manufacturing in a process called *doping*.

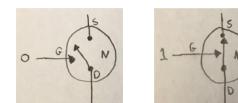
## N-TYPE & P-TYPE SWITCHING TRANSISTORS

- Transistors have 3 connections: source (S), gate (G) and drain(D).
- The connection between the source (S) and the drain (D) “switches” open and closed based on the logic level (i.e. voltages) applied at the gate (G).

In an **N-Type** transistor the switch is open when a 0 is applied at the gate and is closed when a 1 is applied to the gate.




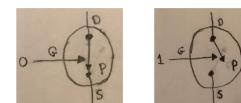In a **P-Type** transistor the switch is closed when a 0 is applied at the gate and is open when a 1 is applied to the gate.



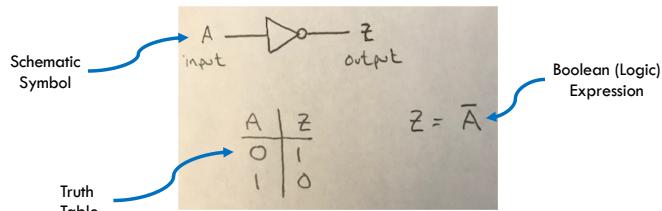
## A NOT GATE ABSTRACTION

- A NOT gate is a circuit that takes a logical value (0 = false or 1 = true) as its input and computes its complement as its output.


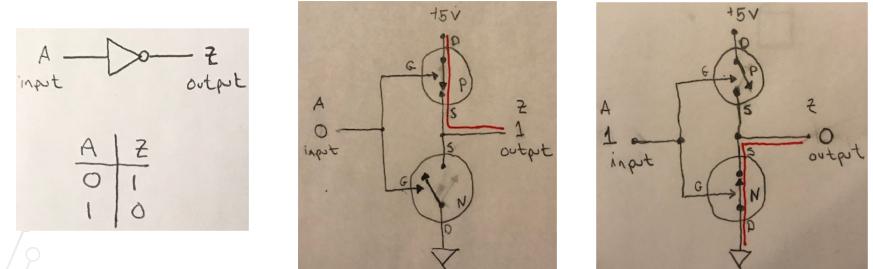
## INSIDE THE NOT GATE ABSTRACTION

- A NOT gate is built using two transistors one P-Type and one N-Type.






Note: The N-Type and P-Type transistors work in a complementary way. When one is open, the other is closed. This is the origins of the term CMOS Technology (Complementary Metal Oxide Semiconductor).

## 2-INPUT LOGIC GATES AS ABSTRACTIONS

- The common 2-input logic gates are:


- AND
- OR
- NAND
- NOR
- XOR
- XNOR

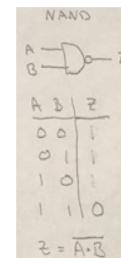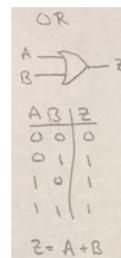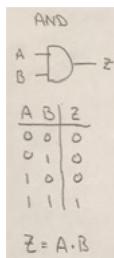
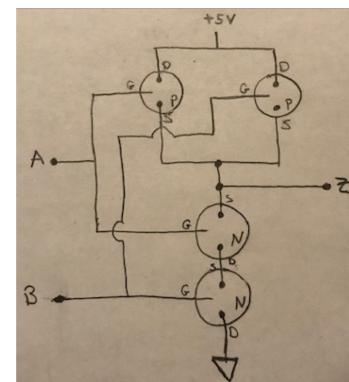
## ACTIVITY



- What 2-input logic function is implemented by this circuit?

Note: For technical reasons P-Type transistors should always be on the +5V side of the circuit (top) and N-Type should always be on the ground side (bottom).



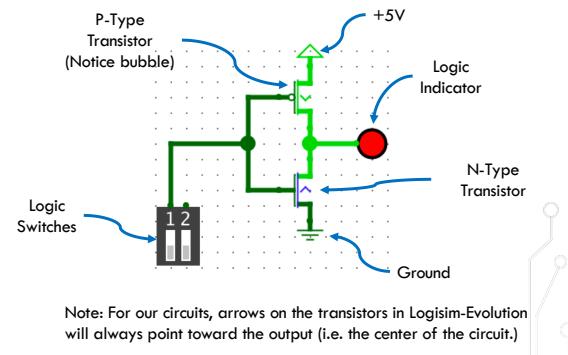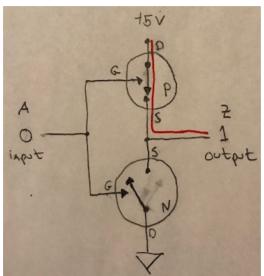
## LOGISIM-EVOLUTION

- Logisim-Evolution is a program that is able to simulate electronic circuits.
  - Download link and instruction are on the course home page.




## LOGISIM-EVOLUTION: FINDING PARTS

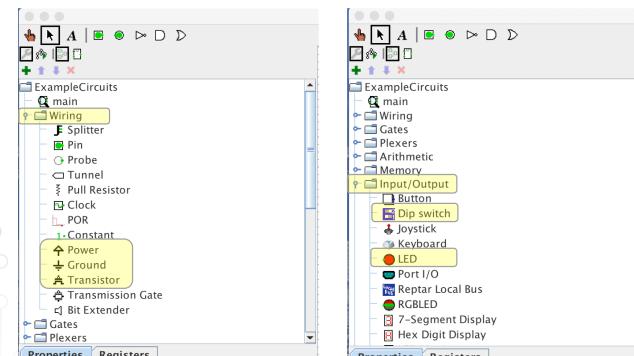

Run & interact with simulation tool  
Build and wire circuits tool.
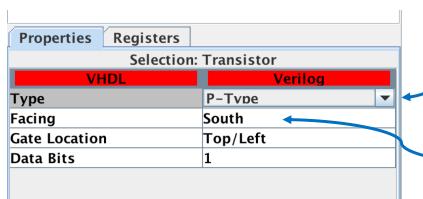
## LOGISIM-EVOLUTION: COMPONENT PROPERTIES

- Click a component to bring up its properties in the lower left panel.
  - Example below is from a transistor.
  - Others are similar.
  - Play around, experiment, explore a bit.



Choose N-Type or P-Type From Dropdown  
Most components can face N, S, E, W. Change orientation to make wiring cleaner.

## ACTIVITY

- Use Logisim-Evolution to build and simulate a NOT gate using transistors.

